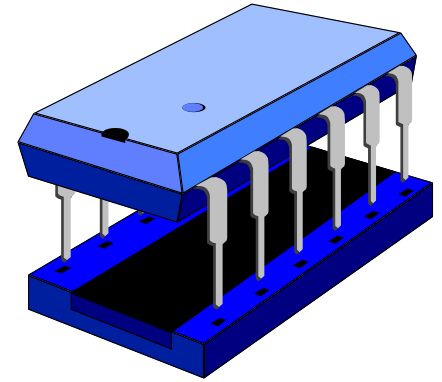


# BASIC CIRCUITS AND MEMORY



---

**Anandha Gopalan** (with thanks to **N. Dulay** and **E. Edwards**)

[axgopala@imperial.ac.uk](mailto:axgopala@imperial.ac.uk)

# Digital Circuits

- Basic Circuits
  - Half Adder
  - Full Adder
  - Latches


# Adders

- A digital circuit that performs addition of numbers
- Not only used in arithmetic logic unit(s), but also in other parts of the processor, where they are used to calculate addresses, table indices, and similar operations
- Most common adders operate on binary numbers

# Half Adder

- Consider adding two 1-bit binary numbers together:

	0	0	1	1
+	0	1	0	1
	00	01	01	10



- Input – 2 separate lines
- Output – two bits – how do we represent this?
  - Use two separate lines (Sum and Carry)

# Half Adder

- Can we now draw the circuit?
  - What do we need? – Truth Tables
    - One each for sum and carry

# Half Adder

- Recall

	0	0	1	1
+	0	1	0	1
	00	01	01	10

- Truth Table

A	B	A + B	Sum	Carry
0	0	0	0	0
0	1	1	1	0
1	0	1	1	0
1	1	2	0	1

What do these correspond to?

# Half Adder

- Selecting Gates

Sum	Carry
0	0
1	0
1	0
0	1




XOR	And
0	0
1	0
1	0
0	1

- Hence, we can build the expressions as:

- Sum =  $A \oplus B$
- Carry =  $A \cdot B$

# Half Adder

- Circuit

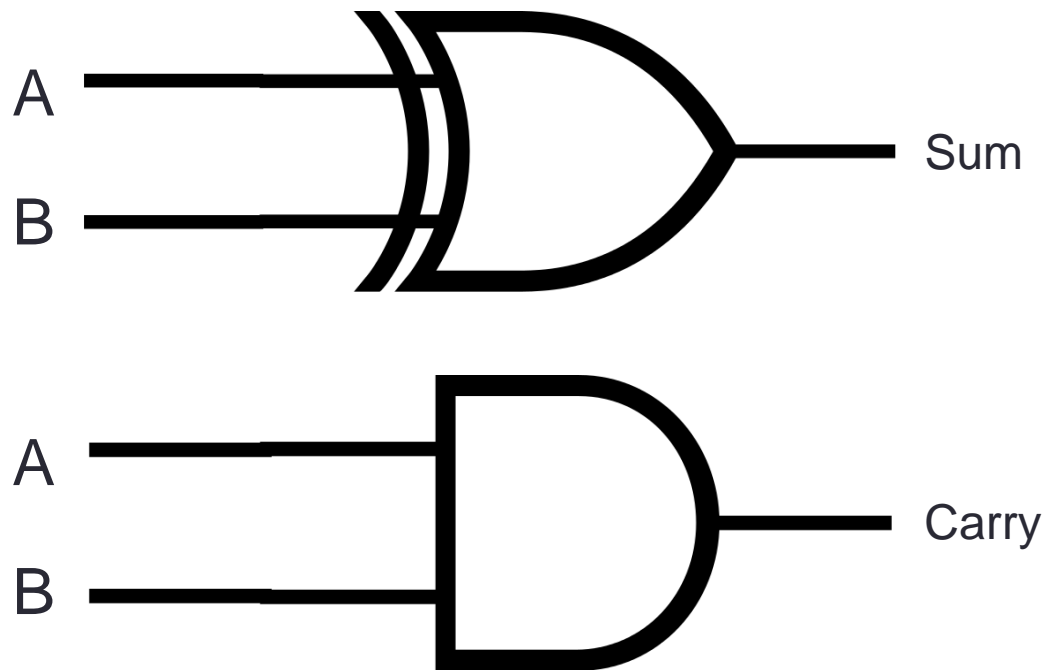


Is this Correct?



# Half Adder


- A more concise and better version 😊

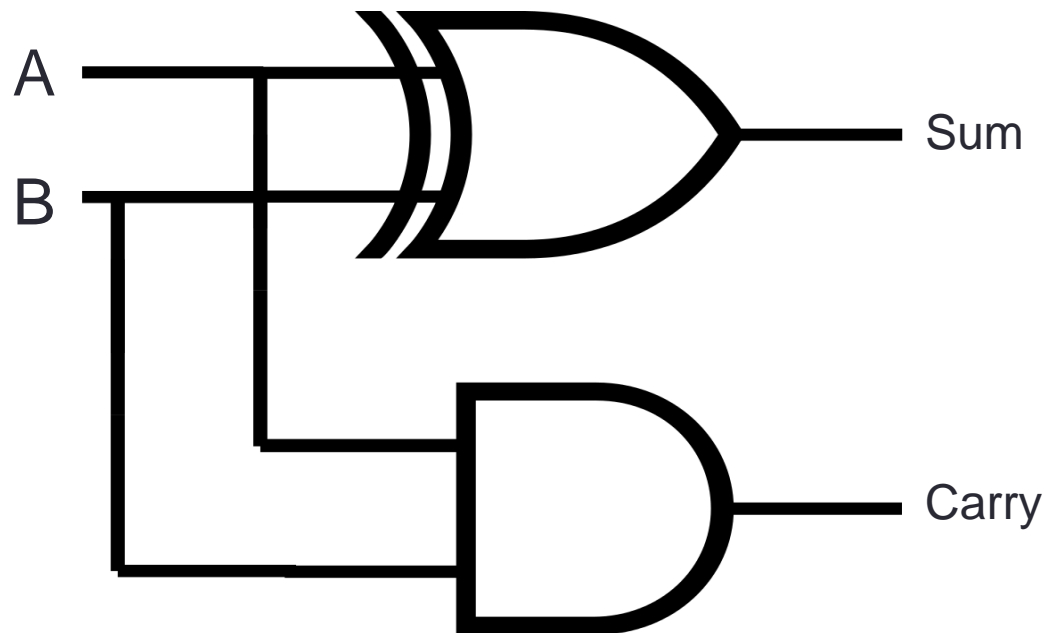

# Full Adder


- Half-adders have a major limitation
  - Cannot accept a carry bit from a previous stage → they cannot be chained together to add multi-bit numbers
- Full-adders can accept three bits as input
  - Third bit is the carry-in bit
- Can be cascaded to produce adders of any number of bits by daisy-chaining the carry of one output to the input of the next

# Full Adder

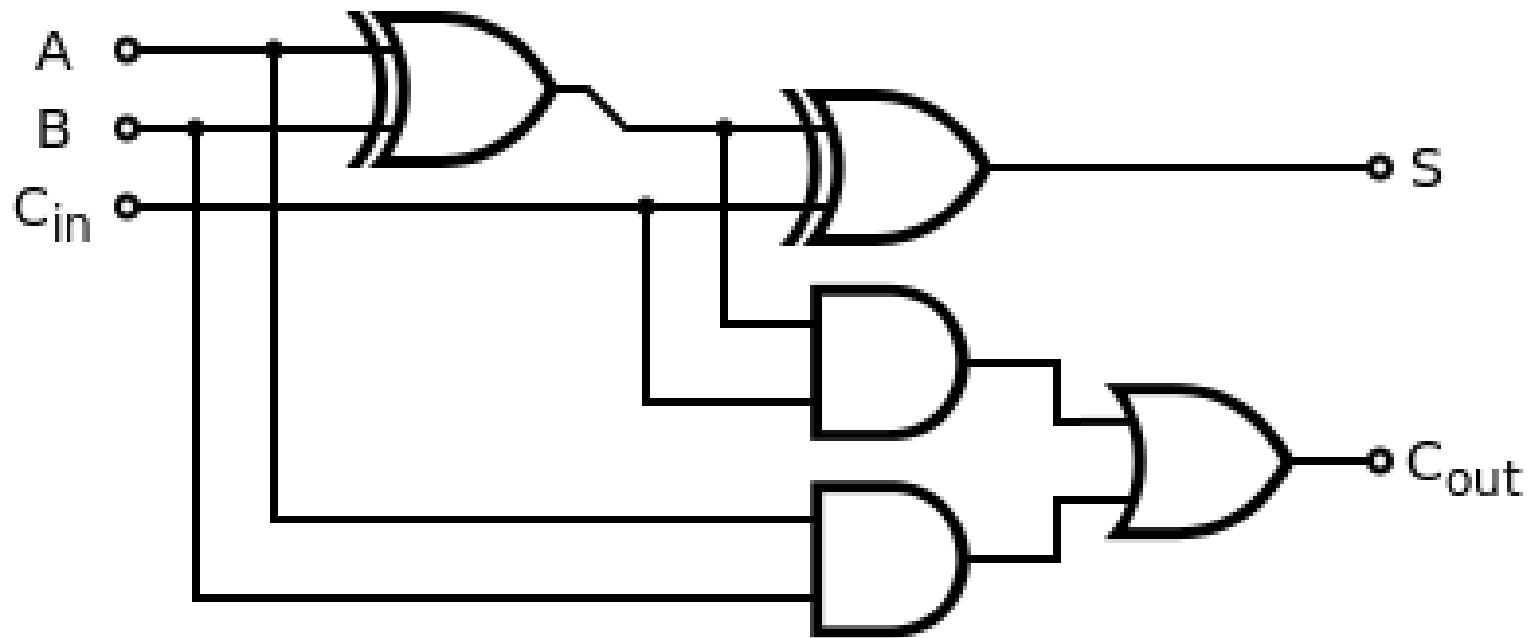

# Full Adder

- Conceptually

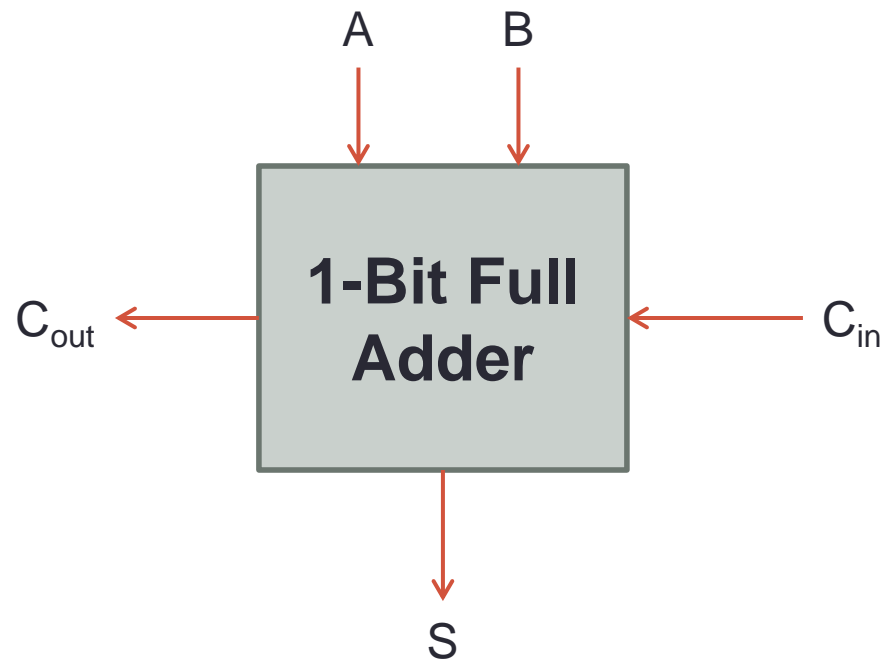


# Ripple-Carry Adder

- Consists of several full adders connected in a series so that the carry must propagate through every full adder before the addition is complete
- Require the least amount of hardware of all adders, but they are the slowest
  - Carry-Lookahead Adder
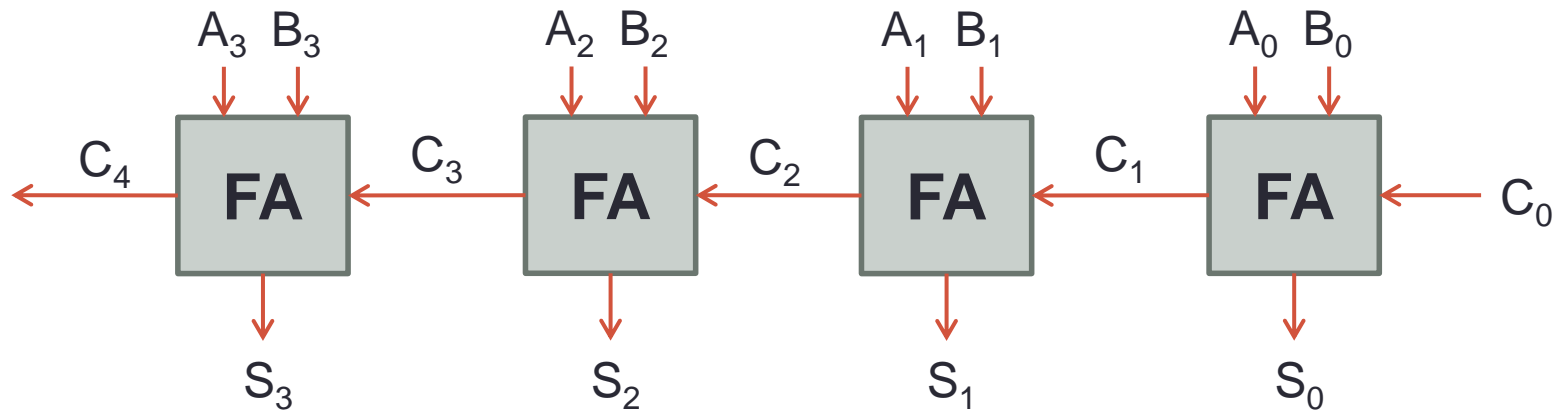
# Ripple-Carry Adder

- The following diagram shows a four-bit adder, which adds the numbers  $A$  and  $B$ , as well as a carry input, together to produce  $S$  and the carry output



# Gates

- Building blocks for combinatorial circuits
  - Output depends only on current Input
- All gates can be built out of NAND and NOR gates
- What if we would like to store values?
  - Use a *feedback* mechanism where the output values depend indirectly, on themselves


# Latches

- Building blocks to sequential circuits
- Can be built from gates
- Able to remember 1-bit of information 😊
- Useful web-page
  - <http://www.play-hookey.com/digital/sequential/>




# Latches

- SR-latch
  - S = Set
  - R = Reset

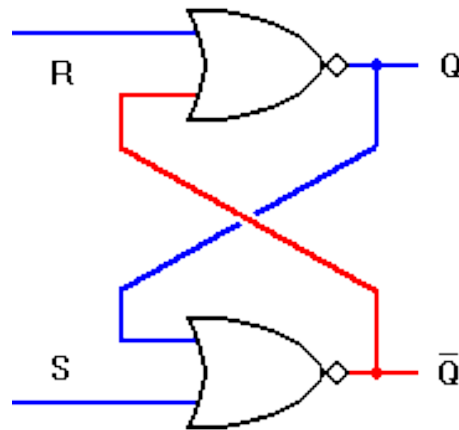

# Latches


- $S = 0, R = 0$

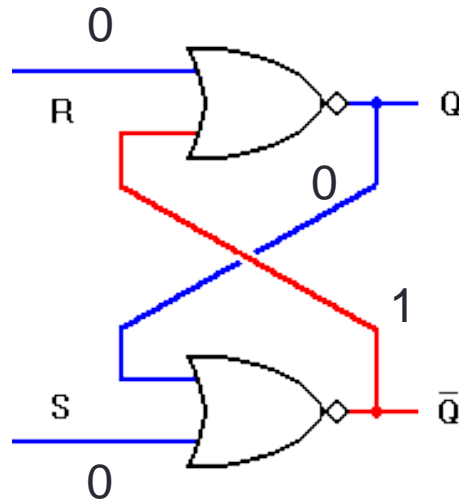

- Value of Q does not change  $\rightarrow$  value is 'remembered'
  - Sometimes called the *latch* state

# Latches


- $S = 1, R = 0$

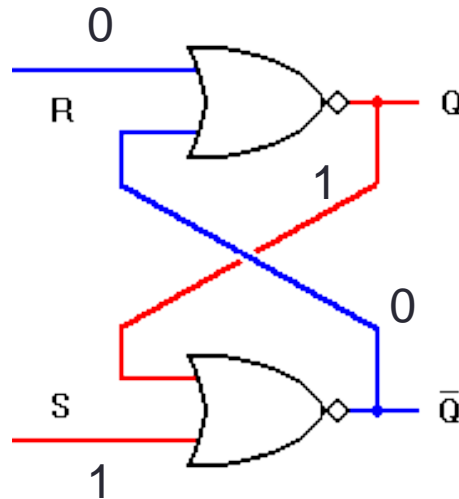

- Set the value of Q

# Latches


- $S = 0, R = 0$

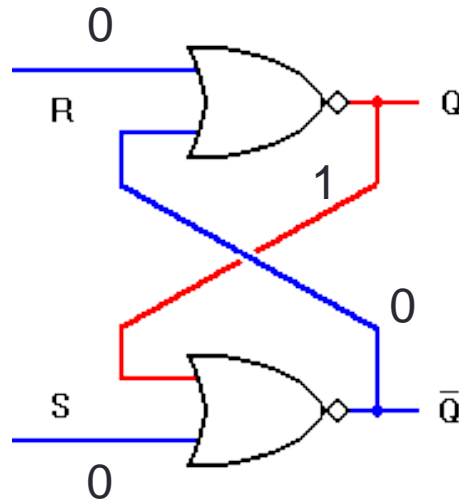

- Value of  $Q$  stays the same – it 'remembers' 😊

# Latches

- $S = 0, R = 1$

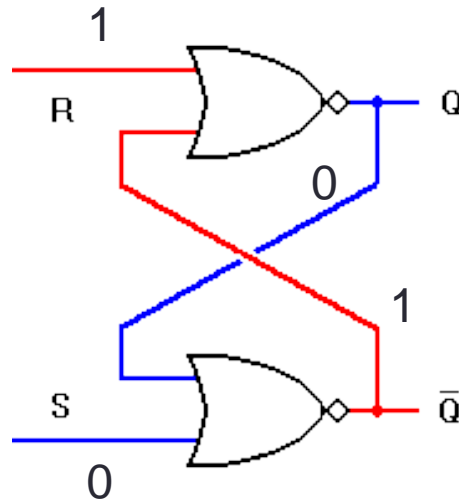

- Reset the value of  $Q$  to 0
- $S = 1, R = 1$  leads to undefined state

# Latches

- SR-Latch: Truth table

S	R	Q	Q'
0	0	Latch	
0	1	0	1
1	0	1	0
1	1	Undefined	

# Flip-Flops

- Latches are *asynchronous* → output changes very soon after the input changes
- Most computers today, are *synchronous*
  - Outputs of all the sequential circuits change simultaneously to the rhythm of a global *clock signal*
- A *flip-flop* is a synchronous version of the latch

# Memory


- Memories hold binary values
  - Data (e.g. Integers, Reals, Characters)
  - CPU Instructions (i.e. Computer Programs)
  - Memory Addresses (“Pointers” to data or instructions)
- Contents remain unchanged unless overwritten with a new binary value
  - Some of them *lose* the content when power is turned off



# Memory – Examples


- CPU, Registers, Caches – L1, L2 [L3]
- Motherboard
  - RAM (Random Access Memory)
  - Caches
  - I/O Registers & Buffers
  - Video-card Memory
- Storage Devices
  - Hard Disks, CDs, DVDs, Tapes, Memory Sticks, Flashcards

# CPU Organisation

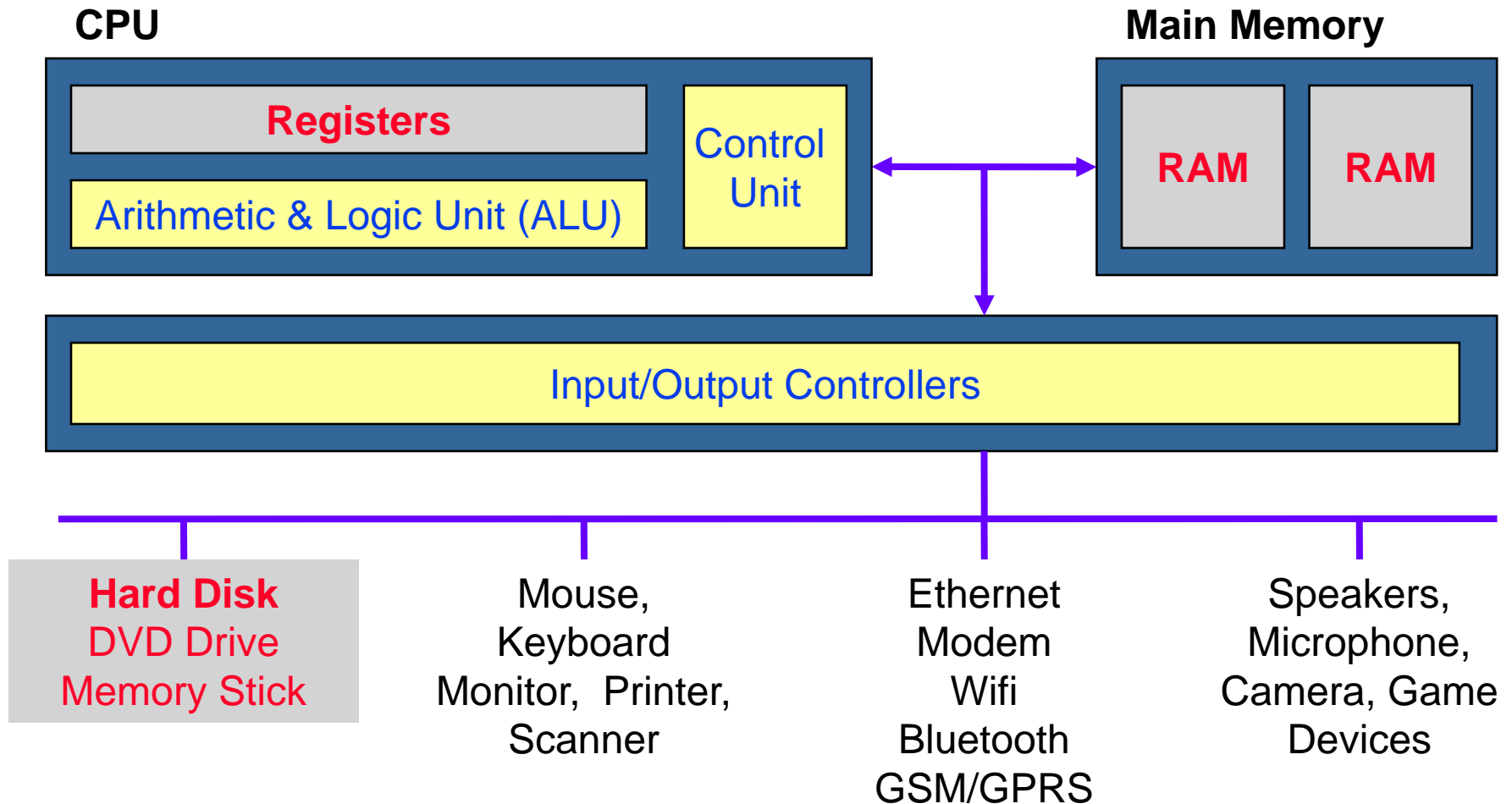


# 3 Types of Memory


CPU

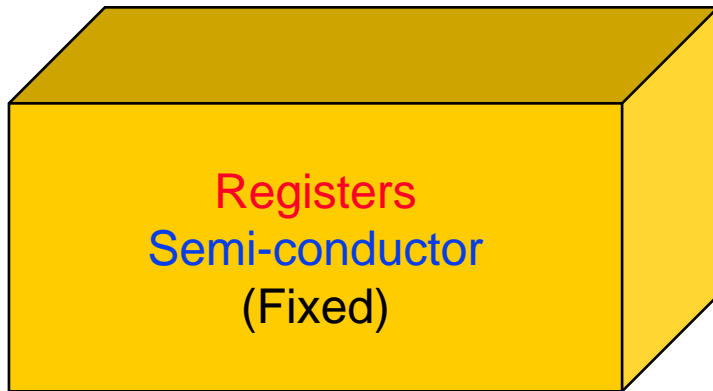

Main Memory

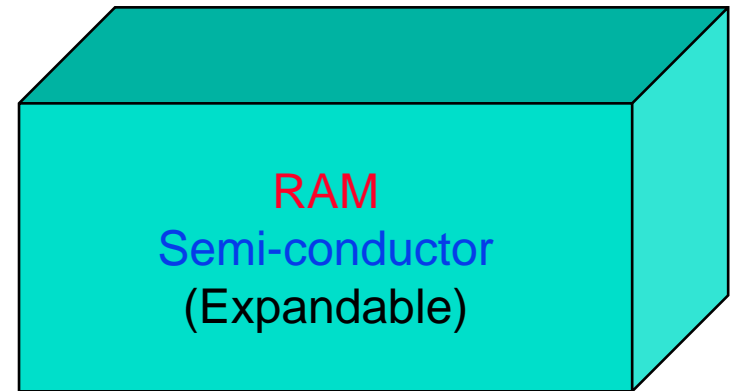

Storage  
Device

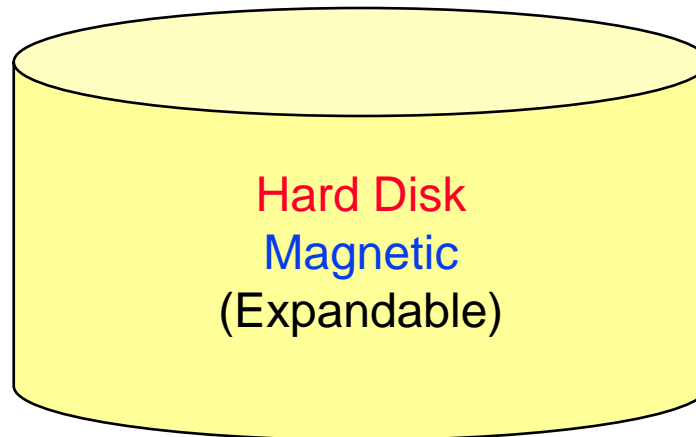


# Capacity


CPU



Main Memory

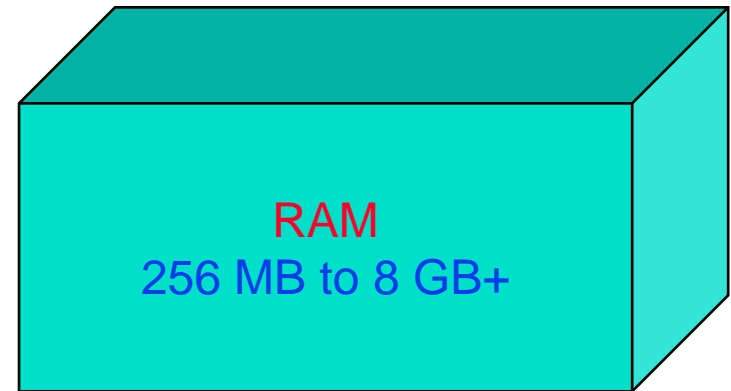

Storage  
Device

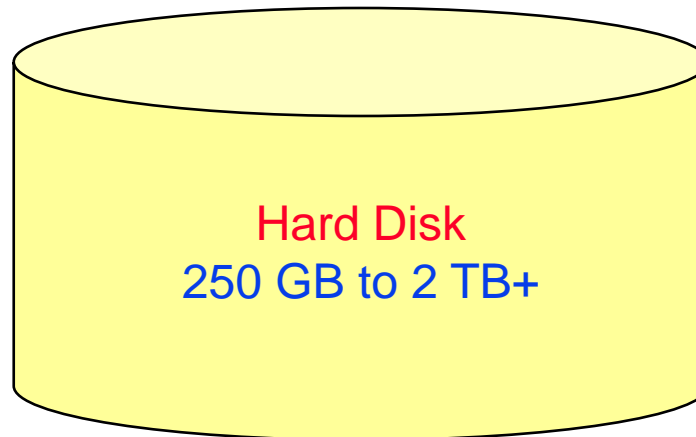

1 KB =  $2^{10}$  bytes


1 MB =  $2^{20}$  bytes

1 GB =  $2^{30}$  bytes


1TB =  $2^{40}$  bytes

# Speed (Access Time)


CPU

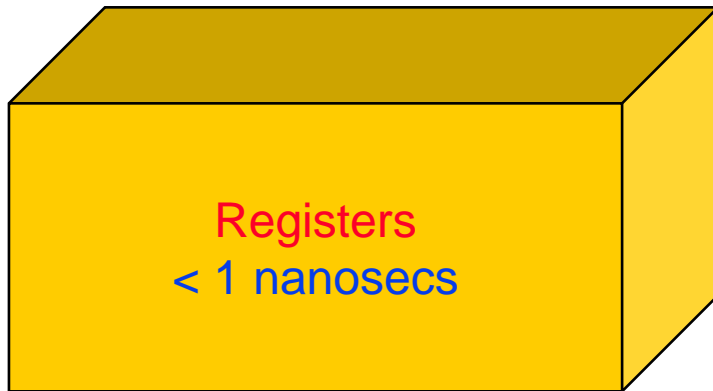

Main Memory

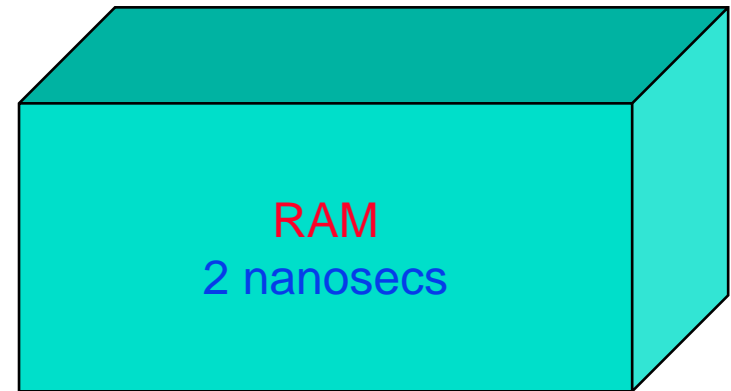


Storage  
Device

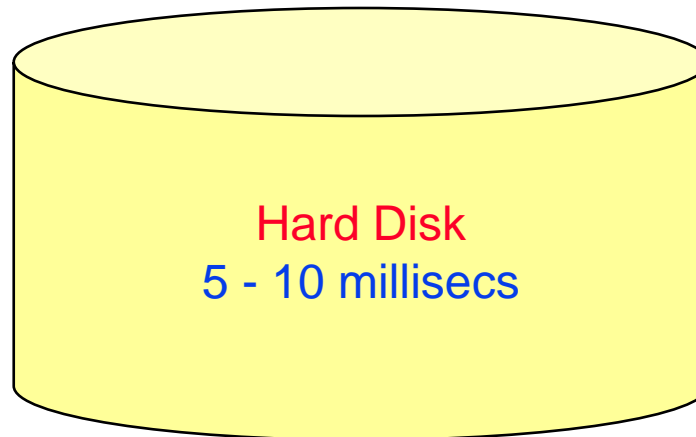

milli =  $10^{-3}$   
micro =  $10^{-6}$   
nano =  $10^{-9}$

# Volatility


CPU

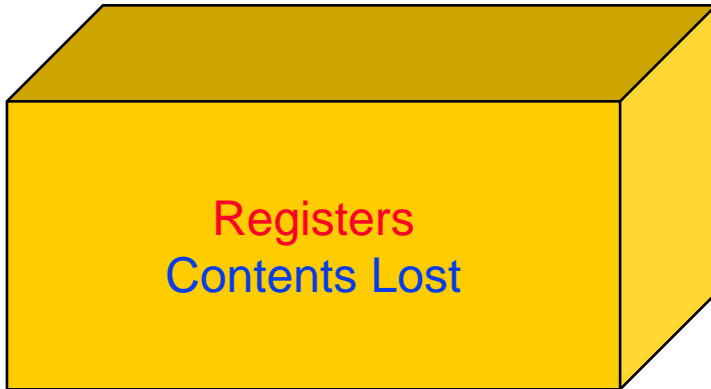

Main Memory




Storage  
Device

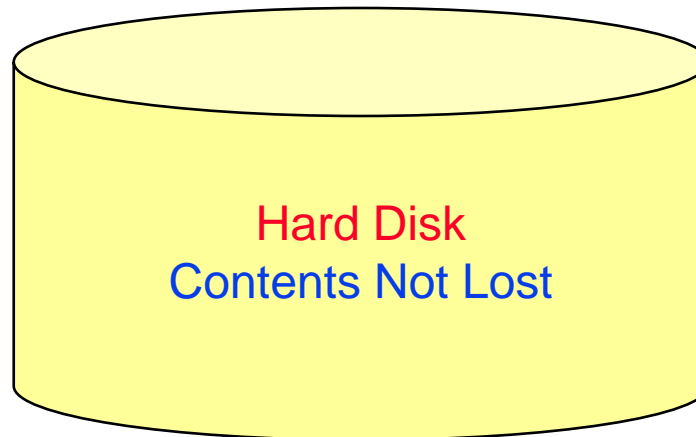


# Cost


CPU

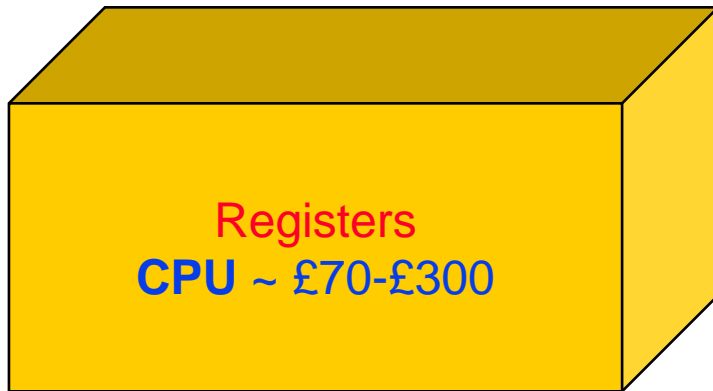

Main Memory

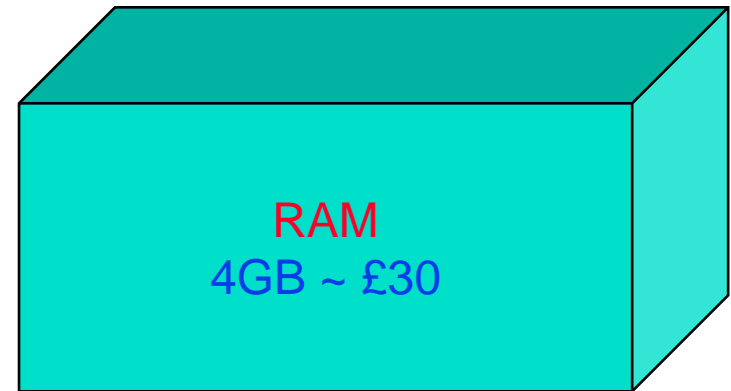

Storage  
Device

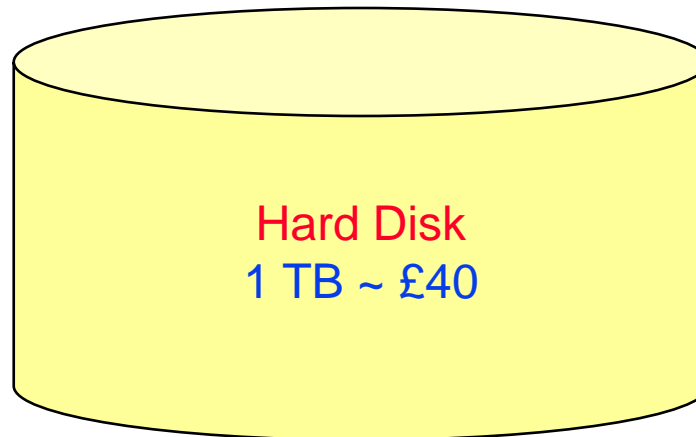

# Summary

